Unified Engineering I

Fall 2006

Problem S3 (Signals and Systems) SOLUTION (Corrected)



1. To begin, we must label each of the elements of the circuit with a polarity (+/-signs) in order to be able to speak about the element voltages. Note that this labeling is arbitrary, so you may get an answer with different signs. I have labeled the elements as above. I have also assigned a ground node, labeled the one known node (V_7) , and labeled the remaining three nodes e_1 , e_2 , and e_3 . Using the node method, the node equations are then, in order,

$$\begin{array}{rrrr} (G_1+G_2+G_5)e_1 & & -G_2e_2 & & -G_5e_3=I_8+G_1V_7 \ (\text{not just } I_8)\\ & & -G_2e_1+(G_2+G_3+G_4)e_2 & & -G_4e_3=0\\ & & -G_5e_1 & & -G_4e_2+(G_4+G_5+G_6)e_3=0 \end{array}$$

Plugging in values, using G = 1/R, we have (leaving out the units)

$$3e_1 - e_2 - e_3 = 8 \pmod{3}$$
$$-e_1 + 1.416\overline{6}e_2 - 0.16\overline{6}e_3 = 0$$
$$-e_1 - 0.16\overline{6}e_2 + 1.416\overline{6}e_3 = 0$$

Solve using a calculator or Matlab or row reduction, we have that

$$e_1 = \frac{40}{7} \text{ V} \approx 5.7143 \text{ V}$$

 $e_2 = \frac{32}{7} \text{ V} \approx 4.5714 \text{ V}$
 $e_3 = \frac{32}{7} \text{ V} \approx 4.5714 \text{ V}$

The element voltages are then found by differencing node potentials:

$$v_{1} = V_{7} - e_{1} = -\frac{5}{7} V$$

$$v_{2} = e_{1} - e_{2} = \frac{8}{7} V$$

$$v_{3} = e_{2} - 0 = \frac{32}{7} V$$

$$v_{4} = e_{2} - e_{3} = 0 V$$

$$v_{5} = e_{1} - e_{3} = \frac{8}{7} V$$

$$v_{6} = e_{3} - 0 = \frac{32}{7} V$$

$$v_{7} = 5 V$$

$$v_{8} = 0 - e_{1} = -\frac{40}{7} V$$

The currents are found from the constitutive relations:

$$i_{1} = \frac{v_{1}}{R_{1}} = -\frac{5}{7} \text{ A}$$

$$i_{2} = \frac{v_{2}}{R_{2}} = \frac{8}{7} \text{ A}$$

$$i_{3} = \frac{v_{3}}{R_{3}} = \frac{8}{7} \text{ A}$$

$$i_{4} = \frac{v_{4}}{R_{4}} = \frac{0}{7} \text{ A}$$

$$i_{5} = \frac{v_{5}}{R_{5}} = \frac{8}{7} \text{ A}$$

$$i_{6} = \frac{v_{6}}{R_{6}} = \frac{10}{7} \text{ A}$$

$$i_{8} = I_{8} = 3 \text{ A}$$

To find i_7 , we must apply KCL at the V_7 node, which implies that $i_7 + i_1 = 0$, so that $i_7 = 5/7$ A.

2. The net power is

$$\sum_{n=1}^{8} i_n v_n = \left(\frac{-5}{7} \cdot \frac{-5}{7} + \frac{8}{7} \cdot \frac{8}{7} + \frac{8}{7} \cdot \frac{32}{7} + 0 \cdot 0 + \frac{8}{7} \cdot \frac{8}{7} + \frac{8}{7} \cdot \frac{32}{7} + \frac{-5}{7} \cdot 5 + 3 \cdot \frac{-40}{7}\right) W = 0 W$$

which is zero by direct calculation.